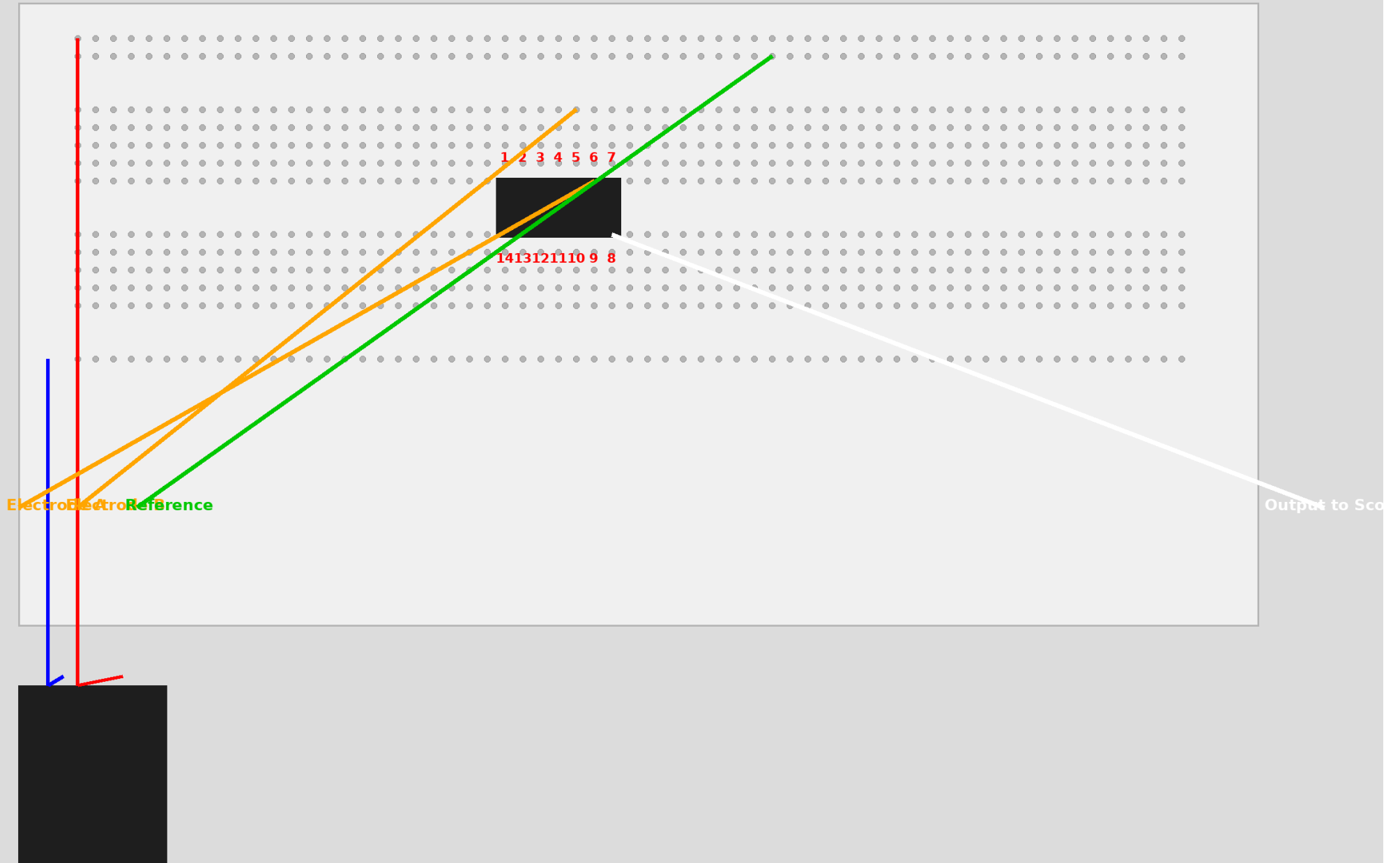


DIY EEG Circuit Guide

EEG Breadboard Layout with External Wires



DIY EEG Circuit Guide

DESIGN.md

EEG Circuit Design (Single TL074, Single 9V Battery)

Architecture

1. Virtual Ground (VGND): 4.5V reference using two 10k resistors and a 100uF capacitor.
2. Stage 1: Instrumentation Amplifier: 3-op-amp InAmp, Gain ~21.
3. Stage 2: 50Hz Notch Filter: Passive Twin-T, tuned for 49.8Hz.
4. Stage 3: Gain + Bandpass Filter: Gain ~471, Bandpass 3.4Hz - 34Hz.

Total Gain: ~10,000.

Component List

- 1x TL074CN IC
- 1x 9V Battery
- Resistors: 2x 1k, 8x 10k, 4x 47k, 1x 470k, 1x 1M.
- Capacitors: 4x 68n, 1x 10n, 1x 100n, 1x 47uF, 1x 100uF.

DIY EEG Circuit Guide

ASSEMBLY.md

Breadboard Assembly Guide

Step 1: Power & VGND

- Red Rail: +9V. Blue Rail: 0V.
- VGND: Junction of two 10k resistors between +9V and 0V. Stabilize with 100uF to 0V.

Step 2: TL074 IC

- Side 1 (Bottom): Pins 1-7. Side 2 (Top): Pins 14-8.
- Pin 4 to +9V. Pin 11 to 0V.

Step 3: Stages

- Stage 1 (InAmp): Pins 12, 13, 14, 5, 6, 7, 2, 3, 1.
- Stage 2 (Notch): Pin 1 to Input, Output to Pin 10.
- Stage 3 (Gain): Pins 8, 9, 10.

Step 4: Connections

- Electrode A: Pin 12.
- Electrode B: Pin 5.
- Reference: VGND.
- Output: Pin 8.

TESTING.md

Safety & Testing

Safety

1. Battery Only.
2. Oscilloscope Isolation.
3. Reference Grounding.

Testing

- Check VGND (4.5V).
- Short inputs to VGND, check output (Flat line).
- Capture Alpha waves (8-13Hz) with eyes closed.